



# Lösungen

## Thema: Spannungsteiler – Seite 1

### Unbelasteter Spannungsteiler

$$1. U_{20} = U \cdot \frac{R_2}{R_1 + R_2} = 12 \text{ V} \cdot \frac{5,5 \text{ k}\Omega}{1,5 \text{ k}\Omega + 5,5 \text{ k}\Omega} = \mathbf{9,43 \text{ V}}$$

$$2. U_{20} = U \cdot \frac{R_2}{R_1 + R_2} = 15 \text{ V} \cdot \frac{90 \text{ k}\Omega}{25 \text{ k}\Omega + 90 \text{ k}\Omega} = \mathbf{11,74 \text{ V}}$$

$$3. \frac{R_1}{R_2} = \frac{3}{5}; \quad \frac{R_1}{R_2} = \frac{U}{U_{20}} - 1; \quad U_{20} = \frac{U}{\frac{R_1}{R_2} + 1} = \frac{24 \text{ V}}{\frac{3}{5} + 1} = \mathbf{15 \text{ V}}$$

$$4. \text{ a) } U_{AB} = U \cdot \frac{R_{AB}}{R} = 150 \text{ V} \cdot \frac{200 \Omega}{900 \Omega} = \mathbf{33,3 \text{ V}}$$

$$\text{ b) } U_{AC} = U \cdot \frac{R_{AC}}{R} = 150 \text{ V} \cdot \frac{500 \Omega}{900 \Omega} = \mathbf{83,3 \text{ V}}$$

$$\text{ c) } U_{BC} = U \cdot \frac{R_{BC}}{R} = 150 \text{ V} \cdot \frac{300 \Omega}{900 \Omega} = \mathbf{50,0 \text{ V}}$$

$$\text{ d) } U_{BD} = U \cdot \frac{R_{BD}}{R} = 150 \text{ V} \cdot \frac{700 \Omega}{900 \Omega} = \mathbf{116,7 \text{ V}}$$

$$\text{ e) } U_{CD} = U \cdot \frac{R_{CD}}{R} = 150 \text{ V} \cdot \frac{400 \Omega}{900 \Omega} = \mathbf{66,7 \text{ V}}$$

$$5. U_{20} = U \cdot \frac{R_2}{R_1 + R_2} \Rightarrow U = U_{20} \cdot \frac{R_1 + R_2}{R_2} = 6,0 \text{ V} \cdot \frac{2,7 \text{ k}\Omega + 8,1 \text{ k}\Omega}{8,1 \text{ k}\Omega} = \mathbf{8,0 \text{ V}}$$

$$6. \frac{R_1}{R_2} = \frac{U}{U_{20}} - 1 \Rightarrow R_1 = \frac{U \cdot R_2}{U_{20}} - R_2 = \frac{24 \text{ V} \cdot 12 \text{ k}\Omega}{9 \text{ V}} - 12 \text{ k}\Omega = \mathbf{20,0 \text{ k}\Omega}$$

$$7. N \hat{=} R; \quad \text{ a) } N_2 = \frac{N \cdot U_{20}}{U} = \frac{640 \cdot 15 \text{ V}}{24 \text{ V}} = \mathbf{400};$$

$$\text{ b) } N_2 = \frac{640 \cdot 5 \text{ V}}{24 \text{ V}} = \mathbf{133,3}$$

$$\text{ c) } N_2 = \frac{640 \cdot 3 \text{ V}}{24 \text{ V}} = \mathbf{80};$$

$$\text{ d) } N_2 = \frac{640 \cdot 6,3 \text{ V}}{24 \text{ V}} = \mathbf{168}$$

$$8. l \hat{=} R; \quad \text{ a) } l_1 = \frac{l \cdot U_1}{U} = \frac{180 \text{ mm} \cdot 22,5 \text{ V}}{230 \text{ V}} = \mathbf{17,6 \text{ mm}}$$

$$\text{ b) } l_2 = \frac{l \cdot U_2}{U} = \frac{180 \text{ mm} \cdot 75 \text{ V}}{230 \text{ V}} = \mathbf{58,7 \text{ mm}}$$

$$\text{ c) } l_3 = \frac{l \cdot U_3}{U} = \frac{180 \text{ mm} \cdot 90 \text{ V}}{230 \text{ V}} = \mathbf{70,4 \text{ mm}}$$

$$9. \frac{U_{20}}{U} = \frac{N_2}{N}; \quad U_{20} = \frac{230 \text{ V} \cdot 1}{450} = \mathbf{0,511 \text{ V}}$$

$$10. U_{20} = \frac{24 \text{ V} \cdot 1}{380} = \mathbf{63,2 \text{ mV}}$$



# Lösungen

## Thema: Spannungsteiler – Seite 2

### Belasteter Spannungsteiler

1. a)  $R_{2L} = \frac{R_2 \cdot R_L}{R_2 + R_L} = \frac{35 \Omega \cdot 50 \Omega}{35 \Omega + 50 \Omega} = 20,6 \Omega$   
 $U_2 = U \cdot \frac{R_{2L}}{R_1 + R_{2L}} = 30 \text{ V} \cdot \frac{20,6 \Omega}{100 \Omega + 20,6 \Omega} = 5,12 \text{ V}$
- b)  $I_L = \frac{U_2}{R_L} = \frac{5,12 \text{ V}}{50 \Omega} = 0,102 \text{ A}$
2. a) Stellung A:  $\Rightarrow$  Kurzschluss von  $R_{L1}$ ,  $R_{L2}$  und  $R_2 \Rightarrow U_2 = 0 \text{ V}$   
 b) Stellung E:  
 $R_L = \frac{R_{L1} \cdot R_{L2}}{R_{L1} + R_{L2}} = \frac{2,2 \text{ k}\Omega \cdot 1,2 \text{ k}\Omega}{2,2 \text{ k}\Omega + 1,2 \text{ k}\Omega} = 0,78 \text{ k}\Omega$   
 $U_2 = \frac{U}{\frac{R_1 \cdot (R_L + R_2)}{R_L \cdot R_2} + 1} = \frac{6 \text{ V}}{\frac{820 \Omega \cdot (780 \Omega + 390 \Omega)}{780 \Omega \cdot 390 \Omega} + 1} = \frac{6 \text{ V}}{3,15 + 1} = 1,44 \text{ V}$
3. a)  $I_{q1} = q_1 \cdot I_B = 3 \cdot 1,0 \text{ mA} = 3,0 \text{ mA}$   
 $R_2 = \frac{U_2}{I_{q1}} = \frac{0,72 \text{ V}}{3,0 \text{ mA}} = 240 \Omega$   
 $R_1 = \frac{U - U_2}{I_{q1} + I_B} = \frac{12,00 \text{ V} - 0,72 \text{ V}}{3,0 \text{ mA} + 1,0 \text{ mA}} = 2820 \Omega$
- b)  $I_{q2} = q_2 \cdot I_B = 4 \cdot 1,0 \text{ mA} = 4,0 \text{ mA}$   
 $R_2 = \frac{U_2}{I_{q2}} = \frac{0,72 \text{ V}}{4,0 \text{ mA}} = 180 \Omega$   
 $R_1 = \frac{U - U_2}{I_{q2} + I_B} = \frac{12,00 \text{ V} - 0,72 \text{ V}}{4,0 \text{ mA} + 1,0 \text{ mA}} = 2260 \Omega$
- c)  $I_{q3} = q_3 \cdot I_B = 5 \cdot 1,0 \text{ mA} = 5,0 \text{ mA}$   
 $R_2 = \frac{U_2}{I_{q3}} = \frac{0,72 \text{ V}}{5,0 \text{ mA}} = 144 \Omega$   
 $R_1 = \frac{U - U_2}{I_{q3} + I_B} = \frac{12,00 \text{ V} - 0,72 \text{ V}}{5,0 \text{ mA} + 1,0 \text{ mA}} = 1880 \Omega$
- $R_2 = R_L \cdot \frac{U}{U_2} \cdot \left( \frac{U_{20} - U_2}{U - U_{20}} \right) = 250 \Omega \cdot \frac{100 \text{ V}}{20 \text{ V}} \cdot \left( \frac{25 \text{ V} - 20 \text{ V}}{100 \text{ V} - 25 \text{ V}} \right) = 83,3 \Omega$   
 $R_1 = R_2 \cdot \left( \frac{U}{U_{20}} - 1 \right) = 83,3 \Omega \cdot \left( \frac{100 \text{ V}}{25 \text{ V}} - 1 \right) = 83,3 \Omega \cdot 3 = 250 \Omega$
4. a)  $R_1 = \frac{R \cdot 3}{3 + 1} = \frac{280 \Omega \cdot 3}{4} = 210 \Omega$ ;  $R_2 = \frac{R \cdot 1}{3 + 1} = \frac{280 \Omega}{4} = 70 \Omega$
- b)  $U_{20} = \frac{R_2}{R_1 + R_2} \cdot U = \frac{70 \Omega}{280 \Omega} \cdot 24 \text{ V} = 6 \text{ V}$
- c)  $U_2 = \frac{U}{\frac{R_1 \cdot (R_L + R_2)}{R_L \cdot R_2} + 1} = \frac{24 \text{ V}}{\frac{210 \Omega \cdot (200 \Omega + 70 \Omega)}{200 \Omega \cdot 70 \Omega} + 1} = \frac{24 \text{ V}}{4,05 + 1} = 4,75 \text{ V}$
- d)  $I_q = \frac{U_2}{R_2} = \frac{4,75 \text{ V}}{70 \Omega} = 0,068 \text{ A}$       f)  $q = \frac{I_q}{I_L} = \frac{I_q}{U_2/R_L} = \frac{0,068 \text{ A}}{0,0238 \text{ A}} = 2,9$
- e)  $I_L = \frac{U_2}{R_L} = \frac{4,75 \text{ V}}{200 \Omega} = 0,0238 \text{ A}$



# Lösungen

## Thema: Spannungsteiler – Seite 3


5. a)

$\vartheta$ in °C	$R_{\vartheta}$ in k $\Omega$	$R_2 \parallel R_{\vartheta}$ in k $\Omega$	$U_2$ in V
0	32	11,5	5,2
20	12,5	7,4	4,0
40	5,4	4,2	2,6
60	2,5	2,2	1,5
80	1,3	1,2	0,9
100	0,7	0,67	0,52
120	0,4	0,39	0,31

$R_{\vartheta}$  aus Diagramm ablesen:

$$R_{2\vartheta} = \frac{R_2 \cdot R_{\vartheta}}{R_2 + R_{\vartheta}} = \frac{18 \text{ k}\Omega \cdot 32 \text{ k}\Omega}{18 \text{ k}\Omega + 32 \text{ k}\Omega} = 11,5 \text{ k}\Omega$$
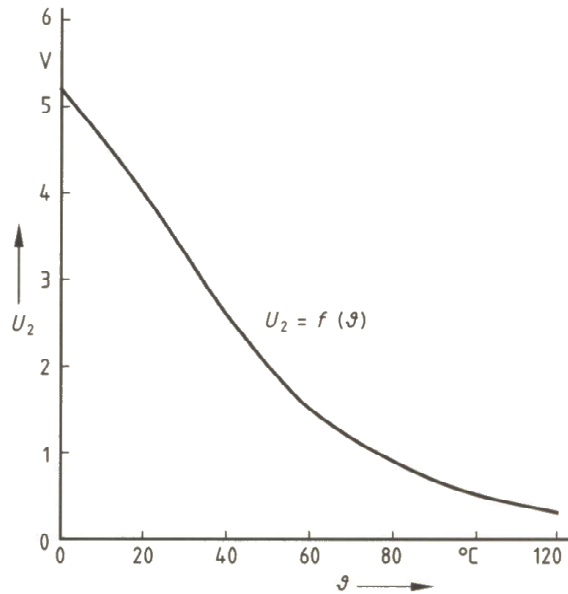
$$U_2 = \frac{U \cdot R_{2\vartheta}}{R_1 + R_{2\vartheta}} = \frac{12 \text{ V} \cdot 11,5 \text{ k}\Omega}{15 \text{ k}\Omega + 11,5 \text{ k}\Omega} = 5,2 \text{ V}$$



6. a) Siehe Schaltskizze

b)  $U_{20} = \frac{R_2}{R_1 + R_2} \cdot U = \frac{6,2 \text{ k}\Omega}{(47 \text{ k}\Omega + 6,2 \text{ k}\Omega)} \cdot 50 \text{ V} = 5,83 \text{ V}$

c) P1:  $R_m = R_L = r_k \cdot U = 666 \frac{\Omega}{\text{V}} \cdot 6 \text{ V} = 4 \text{ k}\Omega$


$$U_2 = \frac{U}{\frac{R_1 \cdot (R_L + R_2)}{R_L \cdot R_2} + 1} = \frac{50 \text{ V}}{\frac{47 \text{ k}\Omega \cdot (4 \text{ k}\Omega + 6,2 \text{ k}\Omega)}{4 \text{ k}\Omega \cdot 6,2 \text{ k}\Omega} + 1} = 2,46 \text{ V}$$

P2:  $R_m = R_L = r_k \cdot U = 3333 \frac{\Omega}{\text{V}} \cdot 6 \text{ V} = 20000 \Omega = 20 \text{ k}\Omega$

$$U_2 = \frac{50 \text{ V}}{\frac{47 \text{ k}\Omega \cdot (20 \text{ k}\Omega + 6,2 \text{ k}\Omega)}{20 \text{ k}\Omega \cdot 6,2 \text{ k}\Omega} + 1} = 4,57 \text{ V}$$

P3:  $R_m = R_L = r_k \cdot U = 20 \frac{\text{k}\Omega}{\text{V}} \cdot 6 \text{ V} = 120 \text{ k}\Omega$
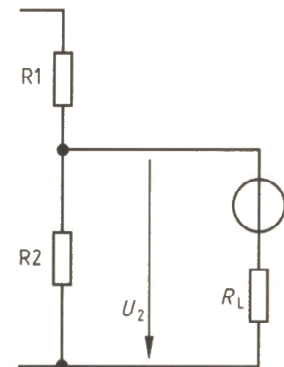
$$U_2 = \frac{50 \text{ V}}{\frac{47 \text{ k}\Omega \cdot (120 \text{ k}\Omega + 6,2 \text{ k}\Omega)}{120 \text{ k}\Omega \cdot 6,2 \text{ k}\Omega} + 1} = 5,57 \text{ V}$$



d) Messfehler bei P1:  $\Delta U = U_{20} - U_2 = 5,83 \text{ V} - 2,46 \text{ V} = 3,37 \text{ V}$

$$\Delta U_{\%} = \frac{3,37 \text{ V} \cdot 100\%}{5,83 \text{ V}} = 58\%$$

bei P2:  $\Delta U = U_{20} - U_2 = 5,83 \text{ V} - 4,57 \text{ V} = 1,26 \text{ V}; \quad \Delta U_{\%} = \frac{1,26 \text{ V} \cdot 100\%}{5,83 \text{ V}} = 22\%$

bei P3:  $\Delta U = U_{20} - U_2 = 5,83 \text{ V} - 5,57 \text{ V} = 0,26 \text{ V}; \quad \Delta U_{\%} = \frac{0,26 \text{ V} \cdot 100\%}{5,83 \text{ V}} = 4,5\%$